



SEQUENTIAL CIRCUITS - III

DESIGN METHOD FOR SYNCHRONOUS COUNTERS


Design Method - Synchronous Counters

Goal : Given the state diagram of a counter realize it using common FFs (and combinational logic).

  *Example : Design a 3-bit counter having the following state diagram.
Use D FFs.*



3-bit synchronous counter

 

FF outputs are **fed back** to **combinational circuit inputs**.

Combinational circuit outputs D_A , D_B , & D_C are connected to D FF inputs and will **be transferred to the output at next active clock edge**.


Key: Design **combinational circuit** to **take previous counter outputs & produce the next state**.

Systematic design method is similar to that used for FF conversion considered before.

Design Method : Steps

Step 1


 
- Draw a **State Diagram** for the desired **Count Sequence**



Step 2

- Determine the **Functional Block Diagram** of the **N-bit Counter**.

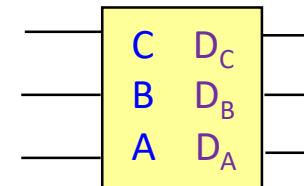 - Number of flip-flops?
- Inputs and Outputs of combinational circuit?



Combinational Circuit

Inputs: Present-state counter outputs (A, B, C).

Outputs: Next-state counter outputs to connect to FF inputs. (D_A, D_B, D_C)

Design Method – Cont'd


Step 3A

- Truth table of the combinational circuit.

A. Determine **next state table** for the counter.

Present-state outputs			Next-state outputs		
C	B	A	C^+	B^+	A^+
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Next-State Table

 

A **synchronous counter** can be realized with D FFs or with any other FF

Design Method – Cont'd


*Excitation Table :
Specifies what the FF inputs should be for a specific $Q \rightarrow Q^+$ transition to occur.

Step 3B

- Truth table of the combinational circuit.
B. Using the excitation table, determine the output values of the combinational circuit.

Present-state outputs			Next-state outputs			Required FF input		
C	B	A	C^+	B^+	A^+	D_C	D_B	D_A
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0

Next-State Table

 


D Flip Flop
Excitation Table

Q	Q^+	D
0	0	0
0	1	1
1	0	0
1	1	1

$$D \Leftrightarrow Q^+$$

 We now have a truth table for the combinational circuit!



Design Method – Cont'd

Step 4

- Realize the circuit.

Present-state outputs			Required FF input		
C	B	A	D _C	D _B	D _A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

BA	C	0	1
00	0	1	(1)
01	0	1	(1)
11	(1)	0	
10	0	1	

$$D_C = ABC\bar{C} + \bar{B}C + \bar{A}C$$


BA	C	0	1
00	0	0	
01	(1)	1	(1)
11	0	0	
10	(1)	1	

$$D_B = A\bar{B} + \bar{A}B = A \oplus B$$

BA	C	0	1
00	(1)	1	(1)
01	0	0	
11	0	0	
10	(1)	1	(1)

$$D_A = \bar{A}$$

Synchronous 3-bit counter

 

Synchronous Counter Example 2

Design a **synchronous counter** with count sequence using DFFs:

101,001,000,010,110,100,101,... (mod-6).

The counter also has an external active high synchronous CLEAR input which will clear the counter to **000** at next active clock edge when set to '1'.

e.g. **101,001,000,010,110,100,000,010..**



1) State Diagram

2) Functional Block Diagram




3) Next State Table / Truth table of C.C.

4) Final Implementation

Step1: Write state diagram.

Step2: Determine functional block diagram of counter.

   Step3 : Functional block diagram of combinational circuit.



Step4 : Get TT of combinational circuit using FF excitation table.

Step5 : Realize circuit.

CLEAR	C	B	A	C ⁺			D _C		
				B ⁺	A ⁺		D _B	D _A	
0	0	0	0	0	1	0	0	1	0
0	0	0	1	0	0	0	0	0	0
0	0	1	0	1	1	0	1	1	0
0	0	1	1	X	X	X	X	X	X
0	1	0	0	1	0	1	1	0	1
0	1	0	1	0	0	1	0	0	1
0	1	1	0	1	0	0	1	0	0
0	1	1	1	X	X	X	X	X	X
1	X	X	X	0	0	0	0	0	0

SOP for flip-flop inputs

$$D_C = \overline{CLEAR} \bullet B + \overline{CLEAR} \bullet C \bullet \overline{A}$$

$$D_B = \overline{CLEAR} \bullet \overline{C} \bullet \overline{A}$$

$$D_A = \overline{CLEAR} \bullet C \bullet \overline{B}$$